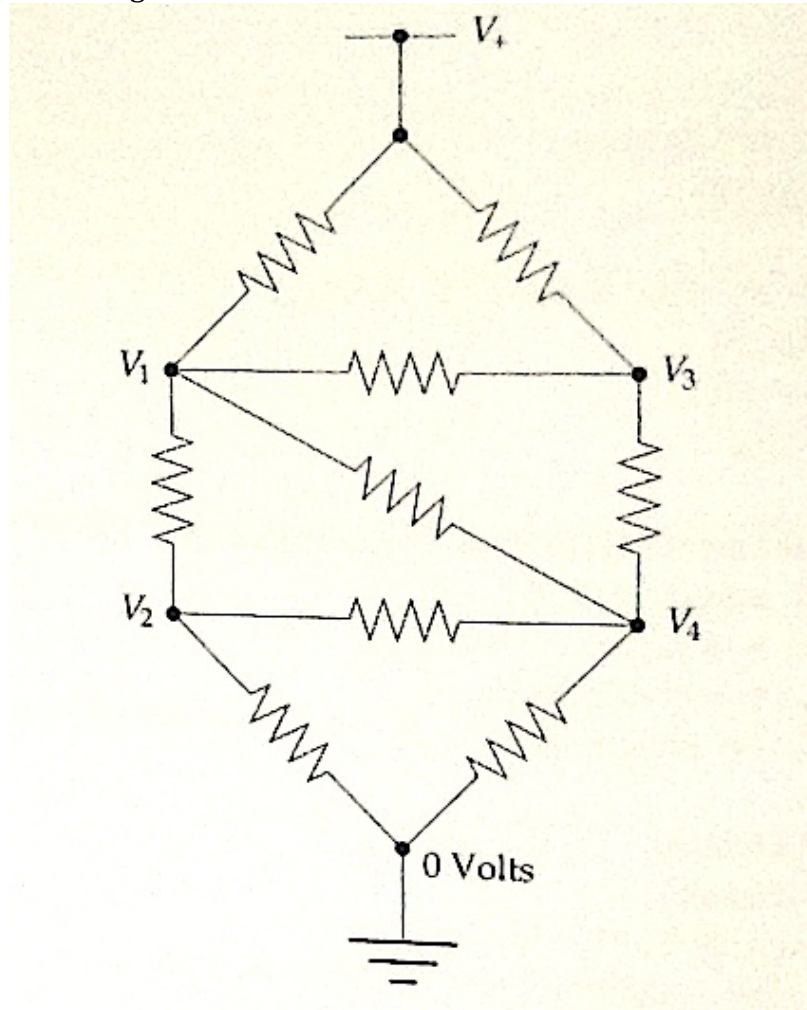


1) Consider the following circuit of resistors:



All the resistors have the same resistance R . The power rail at the top is at voltage $V_+=5V$. What are the other four voltages, V_1 to V_4 ?

Applying Kirchhoff's current law to the junction at V_1 and using Ohm's law ($V=RI$), we have:

$$\frac{V_1 - V_+}{R} + \frac{V_1 - V_3}{R} + \frac{V_1 - V_4}{R} + \frac{V_1 - V_2}{R} = 0$$

or equivalently:

$$4V_1 - V_2 - V_3 - V_4 = V_+$$

- Write similar equations for all the other three junctions with unknown voltages.
- Write a program to solve the four resulting equations using Gaussian elimination and hence find the four voltages.